



required arrival time is 1.9 ns

You need to submit both hardcopy and electronic copy.

The input signal is a unit step, the voltage switches from “1” to “0” at 1ns. The required arrival time for all primary output load is 1.9n. You will need to insert buffers to achieve this.

In this assignment, we are using 45nm high performance CMOS model.

Here is the link: http://ptm.asu.edu/modelcard/HP/45nm_HP.pm

You need download it and include it in your Hspice netlist file (filename.sp)

Use “.include ./cmos45nm_PTM_HP “ to include your downloaded model;

Here is the buffer definition for this assignment

Buf

.MACRO buf16 IN OUT VDD VSS L=45n W=45n

*M0p N1 IN VDD VDD PMOS L=L W='16*W'*

*M0n N1 IN VSS VSS NMOS L=L W='16*W'*

*M1p OUT N1 VDD VDD PMOS L=L W='32*W'*

*M1n OUT N1 VSS VSS NMOS L=L W='32*W'*

.EOM

Use the following command to insert this buffer

“x1 input_node output_node VCC 0 buf16”

X means it's a circuit block;

VCC is the voltage source node;

0 is the default ground node;

Buf16 is the circuit block name;

As for elmore delay calculation:

$$R_{inv} = 18k$$

$$C_{buf} = 2f$$

$$R_{buf} = 0.5k$$

$$D_{buf} = 20ps$$